

# Chapter 3

## Electrical basics lab

1. Calculate the voltage developed across a  $6\text{ k}\Omega$  resistor with  $105\text{ mA}$  flowing through it.
2. The current on a server PSU's  $5\text{ V}$  rail is measured as  $4\text{ A}$ . What power is being delivered by the PSU?
3. Write an expression for  $P$  using only  $R$  and  $I$ .
4. A load consumes  $60\text{ W}$  of power from a  $12\text{ V}$  battery. Calculate the current.
5. The AC mains supply in Ireland has a frequency of  $50\text{ Hz}$ . Calculate the period of the AC waveform.
6. Trains in parts of Europe are supplied with  $15\text{ kV AC}$  at  $16\frac{2}{3}\text{ Hz}$ . How often does the AC cycle repeat?
7. An unknown mains supply is measured to be sinusoidal with an amplitude of  $339.4\text{ V}$  and a frequency of  $50\text{ Hz}$ . Describe this supply in the conventional form.